

(Please write your Exam Roll No.)

.....

Exam Roll No.

.....

END TERM EXAMINATION

FIRST SEMESTER [MCA] DECEMBER-2008

Paper Code: MCA 103

Subject: Digital Electronics

Paper Id: 44103
2008)

(Batch: 2004-

Time: 3 Hours

Maximum Marks: 60

Note: Q. 1 is compulsory. Attempt one question from each unit.

Q.1 Answer the following:

- (a) A NOR gate is also referred to as a 'Negative AND gate'. Why? (1)
- (b) Give the maximum positive and negative numbers which can be represented in 2's complement form using n bits? (1)
- (c) Most PC-compatible computer system use 20-bit address code to identify over one million binary locations. How many hex-characters are required to identify the address (1)
- (d) The logic expression $Y = \prod M(1,4,6,9,10,11,14,15)$ is equivalent to___ (1)
- (e) How many states does a twisted ring counter consists of four flip-flops have? (1)
- (f) Name three major categories into which programmable ROMs can be divided. (1)
- (g) How does a priority encoder differ from an ordinary encoder? (1)
- (h) What do you understand by system bus? (1)
- (i) Why should the shift register stages be edge triggered? (1)
- (j) Design a mod-3 binary counter? (2)
- (K) Attempt **Any Three** of the following: (3 x 3 =9)
 - (i) Explain the operation of Schmitt Trigger work?
 - (ii) Obtain the canonical sum of product and product of sum of the following expression $f = X_1 X_2 X_3 + X_1 X_3 X_4 + X_1 X_2 X_4$

- (iii) Design a 64: 1 multiplexer using 16: 1 multiplexers.
- (iv) Design a parity checker circuit to add an even parity bit to a 16-bit word. Use two 74180 packages.

UNIT - I

- Q2. (a) Discuss the advantages of digital system over analog system. What is the limitation of a digital system? (3)
- (b) Convert the decimal numbers 95.5 into hexadecimal number. (2)
- (c) Write the next four numbers in the following sequence (2)
- (i) Octal counting sequence 124, 125, 126
 - (ii) Hexadecimal sequence E9A, E9B, E9C, E9D
- (d) 7-bit hamming code is received as 1101101. Locate the error position and find the correct code. (2)
- (e) What is the cyclic code? (1)

OR

- Q3. (a) Add the following numbers using the 2's complement method 47 and +29. (3)
- (b) What is the necessary condition for a weighted code to be self-complementing code? Give two examples of weighted code. (2)
- (c) Perform the following subtraction using the 10's complement arithmetic 196-155. (2)
- (d) Design XNOR gate using minimum number of NAND gates only. (3)

UNIT - II

- Q4. (a) Design BCD-to-Excess -3 code converter. (4)
- (b) Reduce the following Boolean expression using Boolean algebra

$$((AB' + ABC) + A(B+AB'))'$$
 (3)
- (c) Design a 3 bit binary-to-octal decoder. (3)

OR

- Q5. (a) Design a combinational circuit with 4 input and outputs. The output generates the 2's complement of the input binary number. (5)
- (b) Using the K-map simplify the following function into minimal SOP
- $$f(u,w,x,y,z) = \sum m(0,2,5,7,9,11,13,15,16,18,21,23,25,27,29,31) \quad (5)$$

UNIT - III

- Q6. (a) Explain the working of Master Slave J-K Flip-Flop. (5)
- (b) How will you convert a D flip flop into a J-K flip flop. (5)

OR

- Q7. (a) Describe the working of shift left register with diagram. (3)
- (b) Design a synchronous decade counter to count in the Excess-3 code sequence. Using minimum number of J-K flip flops. (7)

UNIT - IV

- Q8. (a) Explain the working of R-2R digital-to-analog converter. Discuss the characteristics of D\A converters. (6)
- (b) What is PLD? How are PLD s categorized? Draw the structure of simple PLA of the following function

$$X = A'B'C'D + A'B'CD$$

$$Y = A'B'CD + ABCD'$$

$$Z = A'B'C'D + A'B'CD + ABCD' \quad (4)$$

OR

- Q9. (a) Draw the functional block diagram of 8085 microprocessor. (7)
- (b) Write short notes on **Any One** of the following: (3)
- (i) Content addressable memory
- (ii) 3-bit parallel comparator A/D converter
